

# NIGHT TRAIN

## overdrive





### Night Train Overdrive

Low to mid gain warm sounding overdrive. Based on the NPN-PNP "antiparallel" pair developed and first used in stompbox by Arsenio Novo, idea presented on [rec.music.makers.guitar.newsgroup](http://rec.music.makers.guitar.newsgroup).

After playing with different versions of the circuit i added the following feratures:

- input buffer
- gain control
- simple lowpass tone control
- output buffer

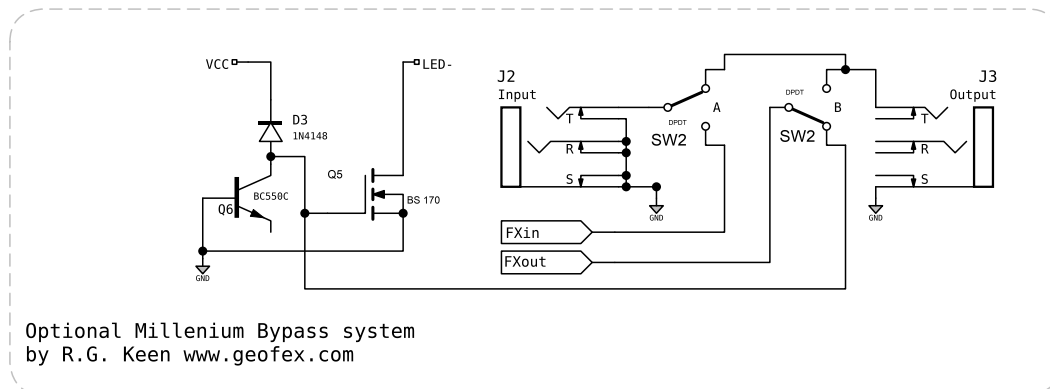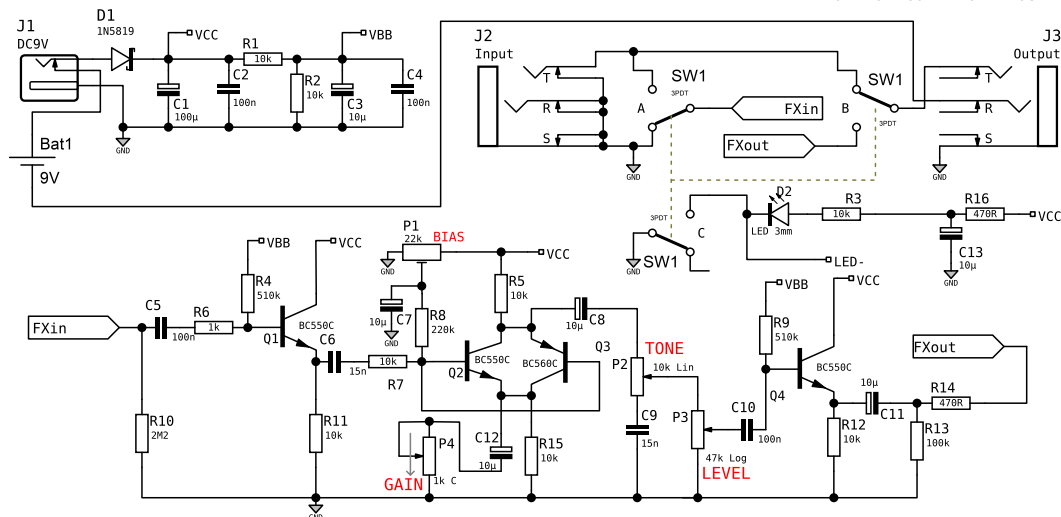(c) 2007/15 Piotr Zapart  
[www.hexeguitar.com](http://www.hexeguitar.com)  
NOT FOR COMMERCIAL USE!



Bias setting: Tweak it until it sounds good!

Bat = 9V

C1 = 100μ (25V RM2.5/6.3)  
C2 = 100n (50V Ceramic)  
C3 = 10μ (50V RM2/5)  
C4 = 100n (50V Ceramic)  
C5 = 100n (MKT 63V RM5mm )  
C6 = 15n (MKT 63V RM5mm )  
C7 = 10μ (50V RM2/5)  
C8 = 10μ (50V RM2/5)  
C9 = 15n (MKT 63V RM5mm )  
C10 = 100n (MKT 63V RM5mm )  
C11 = 10μ (50V RM2/5)  
C12 = 10μ (50V RM2/5)  
C13 = 10μ (50V RM2/5)

D1 = 1N5819 (Schottky diode)  
D2 = LED 3mm ultrabright  
D3 = 1N4148

J1 = DC9V (DC Jack 5.5/2.1mm)  
J2 = Input (Jack TRS switched)  
J3 = Output (Jack TRS switched)

P1 = 22k (PT10 trimpot)  
P2 = 10k Lin (ALPHA 16mm)  
P3 = 47k Log (ALPHA 16mm)  
P4 = 1k C (ALPHA 16mm)

Q1 = BC550C (TO92 CBE)  
Q2 = BC550C (TO92 CBE)  
Q3 = BC560C (TO92 CBE)  
Q4 = BC550C (TO92 CBE)  
Q5 = BS170 (TO92 DGS)  
Q6 = BC550C (TO92 CBE)

R1 = 10k  
R2 = 10k  
R3 = 10k  
R4 = 510k  
R5 = 10k  
R6 = 1k  
R7 = 10k  
R8 = 220k  
R9 = 510k  
R10 = 2M2  
R11 = 10k  
R12 = 10k  
R13 = 100k  
R14 = 470R  
R15 = 10k  
R16 = 470R

SW1 = 3PDT  
SW2 = DPDT (DPDT switch)

Install  
only when  
using  
MILLENNIUM  
BYPASS

This is the main NPN/PNP pair responsible for the overdrive sound. Feel free to experiment with different types.

Watch out the pinout!